LAB 3: Adder and Subtractor Unit

1. Objectives:

- In this lab you will build a 4-bit adder-subtractor unit (ASU).
- · You are asked to prepare and compile a VHDL file to implement the 4-bit ASU.
- The decoded output of the three significant bits of the ASU will consist of a set of four different signals (ABCD-signals), which will be assigned individually. (See page 2 for various examples.)

2. Lab Preparation

- 1) Code a VHDL file to implement the ASU represented.
- 2) Minimize the logic expressions for your customized ABCD-signals. These minimized logic expressions are to be implemented as combinational circuit C in Figure 1 (shown below).

 


Figure 1

- 3) Modify the VHDL file obtained in 1) to implement the minimized logic expressions for ABCD signals.
- 4) Using Functional Simulator, verify the circuit described by the VHDL file obtained in 3). Observe the following signals: X3, X2, X1, X0, Y3, Y2, Y1, Y0, S3, S2, S1, S0, Cout, Cin.

Adder-Subtractor Decoded Outputs – Assignment Exercises

| | | S | | Ex.1 | | | | Ex.2 | | | | Ex.3 | | | | Ex.4 | | | | | E | ι.5 | | | Ea | .6 | | Ex.7 | | | |
|---|---|---|---|------|---|---|---|------|---|---|---|------|---|---|---|------|---|---|---|---|---|-----|---|---|----|----|---|------|---|---|---|
| 2 | | 1 | 0 | A | В | С | D | Α | В | С | D | Α | В | C | D | A | В | С | D | A | В | С | D | Α | В | С | D | A | В | C | D |
| 0 | (| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | (| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | (| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

| | S | | | Ex.8 | | | | Ex.9 | | | | Ex.10 | | | | Ex.11 | | | | | Ex | .12 | | | Ex | .13 | | Ex.14 | | | |
|---|---|---|---|------|---|---|---|------|---|---|---|-------|---|---|---|-------|---|---|---|---|----|-----|---|---|----|-----|---|-------|---|---|---|
| | 2 | 1 | 0 | Α | В | С | D | A | В | С | D | Α | В | C | D | Α | В | С | D | Α | В | С | D | Α | В | С | D | A | В | С | D |
| (| 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| (| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| (| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |

| | S | | Ex.15 | | | | | Ex.16 | | | | Ex.17 | | | | Ex.18 | | | | Ex | .19 | | Ex.20 | | | | Ex.21 | | | |
|---|---|---|-------|---|---|---|---|-------|---|---|---|-------|---|---|---|-------|---|---|---|----|-----|---|-------|---|---|---|-------|---|---|---|
| 2 | 1 | 0 | Α | В | С | D | Α | В | С | D | Α | В | С | D | Α | В | С | D | A | В | С | D | Α | В | С | D | Α | В | С | D |
| 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |